

Chapter 7: Hierarchical Structural Modeling

Prof. Ming-Bo Lin

Department of Electronic Engineering

National Taiwan University of Science and Technology

Syllabus

❖ Objectives

❖ Module

- Module definitions
- Parameters
- Module instantiation
- Module parameter values
- Hierarchical path names

❖ Generate statements

- Generate-loop statement
- Generate-conditional statement
- Generate-case statement

Module Definitions

// port list style

```
module module_name [#(parameter_declarations)][port_list];  
parameter_declarations; // if no parameter ports are used  
port_declarations;  
other_declaration;  
statements;  
endmodule
```

// port list declaration style

```
module module_name [#(parameter_declarations)][port_declarations];  
parameter_declarations; // if no parameter ports are used  
other_declarations;  
statements;  
endmodule
```

Port Declarations

❖ Three types

- input
- output
- inout



```
module adder(x, y, c_in, sum, c_out);  
input [3:0] x, y;  
input c_in;  
output reg [3:0] sum;  
output reg c_out;
```

Syllabus

❖ Objectives

❖ Module

- Module definitions
- Parameters
- Module instantiation
- Module parameter values
- Hierarchical path names

❖ Generate statements

Types of Parameters

❖ module parameters

- parameter
- localparam

❖ specify parameters

```
parameter SIZE = 7;  
parameter WIDTH_BUSA = 24, WIDTH_BUSB = 8;  
parameter signed [3:0] mux_selector = 4'b0;
```

Constants Specified Options

❖ `define compiler directive

``define BUS_WIDTH 8`

❖ Parameter

`parameter BUS_WIDTH = 8;`

❖ localparam

`localparam BUS_WIDTH = 8;`

Syllabus

❖ Objectives

❖ Module

- Module definitions
- Parameters
- **Module instantiation**
- Module parameter values
- Hierarchical path names

❖ Generate statements

Module Instantiation

❖ Syntax

```
module_name [#(parameters)]
```

```
    instance_name [range]([ports]);
```

```
module_name [#(parameters)]
```

```
    instance_name [{,instance_name}](ports);
```

Port Connection Rules

❖ Named association

`.port_id1(port_expr1), ..., .port_idn(port_exprn)`

❖ Positional association

`port_expr1, ..., port_exprn`

Syllabus

❖ Objectives

❖ Module

- Module definitions
- Parameters
- Module instantiation
- **Module parameter values**
- Hierarchical path names

❖ Generate statements

Parameterized Modules

❖ An example

```
module adder_nbit(x, y, c_in, sum, c_out);  
parameter N = 4; // set default value  
input [N-1:0] x, y;  
input c_in;  
output [N-1:0] sum;  
output c_out;  
  
assign {c_out, sum} = x + y + c_in;  
endmodule
```

Overriding Parameters

- ❖ Using module instance
parameter value
assignment
--- two parameters

```

module hazard_static (x, y, z, f);
parameter delay1 = 2, delay2 = 5;
...
and #delay2 a1 (b, x, y);
not #delay1 n1 (a, x);
and #delay2 a2 (c, a, z);
or #delay2 o2 (f, b, c);
endmodule

```

```

// define top level module
module ...
...
hazard_static #(4, 8) example (x, y, z, f);


```

```

hazard_static #(.delay2(4), .delay1(6))
example (x, y, z, f);

```

 - parameter value assignment by name ---
minimize the chance of error!



Syllabus

- ❖ Objectives
- ❖ Module
- ❖ Generate statements
 - Generate-loop statements
 - Generate-conditional statements
 - Generate-case statements

generate Block Structures

- ❖ The keywords used
 - generate and endgenerate

```
// convert Gray code into binary code
parameter SIZE = 8;
input [SIZE-1:0] gray;
output [SIZE-1:0] bin;
genvar i;
generate for (i = 0; i < SIZE; i = i + 1) begin: bit
    assign bin[i] = ^gray[SIZE-1:i];
end endgenerate
```

```
parameter SIZE = 8;  
input [SIZE-1:0] gray;  
output [SIZE-1:0] bin;  
begin: bit  
    assign bin[0] = ^gray[7:0];  
    assign bin[1] = ^gray[7:1];  
    assign bin[2] = ^gray[7:2];  
    assign bin[3] = ^gray[7:3];  
    assign bin[4] = ^gray[7:4];  
    assign bin[5] = ^gray[7:5];  
    assign bin[6] = ^gray[7:6];  
    assign bin[7] = ^gray[7:7];  
end
```


The generate Loop Construct

```
// convert Gray code into binary code
parameter SIZE = 8;
input [SIZE-1:0] gray;
output [SIZE-1:0] bin;
reg [SIZE-1:0] bin;

genvar i;
generate for (i = 0; i < SIZE; i = i + 1) begin:bit
    always @(*)
        bin[i] = ^gray[SIZE - 1: i];
end endgenerate
```

```
// convert Gray code into binary code
```

```
parameter SIZE = 8;
```

```
input [SIZE-1:0] gray;
```

```
output [SIZE-1:0] bin;
```

```
reg [SIZE-1:0] bin;
```

```
begin: bit
```

```
    always @(*) bin[0] = ^gray[7: 0];
```

```
    always @(*) bin[1] = ^gray[7: 1];
```

```
    always @(*) bin[2] = ^gray[7: 2];
```

```
    always @(*) bin[3] = ^gray[7: 3];
```

```
    always @(*) bin[4] = ^gray[7: 4];
```

```
        :      :      :
```

```
    always @(*) bin[7] = ^gray[7: 7];
```

```
end endgenerate
```

Syllabus

- ❖ Objectives
- ❖ Module
- ❖ Generate statements
 - Generate-loop statements
 - **Generate-conditional statements**
 - Generate-case statements

An n -bit Adder

```
// define a full adder at dataflow level.  
module full_adder(x, y, c_in, sum, c_out);  
// I/O port declarations  
input  x, y, c_in;  
output sum, c_out;  
// Specify the function of a full adder.  
    assign {c_out, sum} = x + y + c_in;  
endmodule
```

An n -bit Adder

```
module adder_nbit(x, y, c_in, sum, c_out);  
...  
genvar i;  
wire [N-2:0] c;    // internal carries declared as nets.  
generate for (i = 0; i < N; i = i + 1) begin: adder  
    if (i == 0)      // specify LSB  
        full_adder fa (x[i], y[i], c_in, sum[i], c[i]);  
    else if (i == N-1) // specify MSB  
        full_adder fa (x[i], y[i], c[i-1], sum[i], c_out);  
    else              // specify other bits  
        full_adder fa (x[i], y[i], c[i-1], sum[i], c[i]);  
end endgenerate
```

An n -bit Adder

```
module adder_nbit(x, y, c_in, sum, c_out);  
...  
genvar i;  
wire [N-2:0] c;    // internal carries declared as nets.  
generate for (i = 0; i < N; i = i + 1) begin: adder  
    if (i == 0)      // specify LSB  
        assign {c[i], sum[i]} = x[i] + y[i] + c_in;  
    else if (i == N-1) // specify MSB  
        assign {c_out, sum[i]} = x[i] + y[i] + c[i-1];  
    else              // specify other bits  
        assign {c[i], sum[i]} = x[i] + y[i] + c[i-1];  
end endgenerate
```

An n -bit Adder

```
module adder_nbit(x, y, c_in, sum, c_out);  
...  
genvar i;  
reg [N-2:0] c;    // internal carries declared as nets.  
generate for (i = 0; i < N; i = i + 1) begin: adder  
    if (i == 0)    // specify LSB  
        always @(*) {c[i], sum[i]} = x[i] + y[i] + c_in;  
    else if (i == N-1) // specify MSB  
        always @(*) {c_out, sum[i]} = x[i] + y[i] + c[i-1];  
    else           // specify other bits  
        always @(*) {c[i], sum[i]} = x[i] + y[i] + c[i-1];  
end endgenerate
```

A Two's Complement Adder


```
module twos_adder_nbit(x, y, mode, sum, c_out);  
  ...  
  genvar i;  
  wire [N-2:0] c;  // internal carries declared as nets.  
  wire [N-1:0] t;  // true/ones complement outputs  
  generate for (i = 0; i < N; i = i + 1) begin:  
    // ones_complement_generator  
    xor xor_ones_complement (t[i], y[i], mode);  
  end endgenerate
```


A Two's Complement Adder

```
generate for (i = 0; i < N; i = i + 1) begin: adder
  if (i == 0)           // specify LSB
    full_adder fa (x[i], t[i], mode, sum[i], c[i]);
  else if (i == N-1) // specify MSB
    full_adder fa (x[i], t[i], c[i-1], sum[i], c_out);
  else                 // specify other bits
    full_adder fa (x[i], t[i], c[i-1], sum[i], c[i]);
end endgenerate
```

A Two's Complement Adder


❖ The RTL schematic from Synplify Pro.

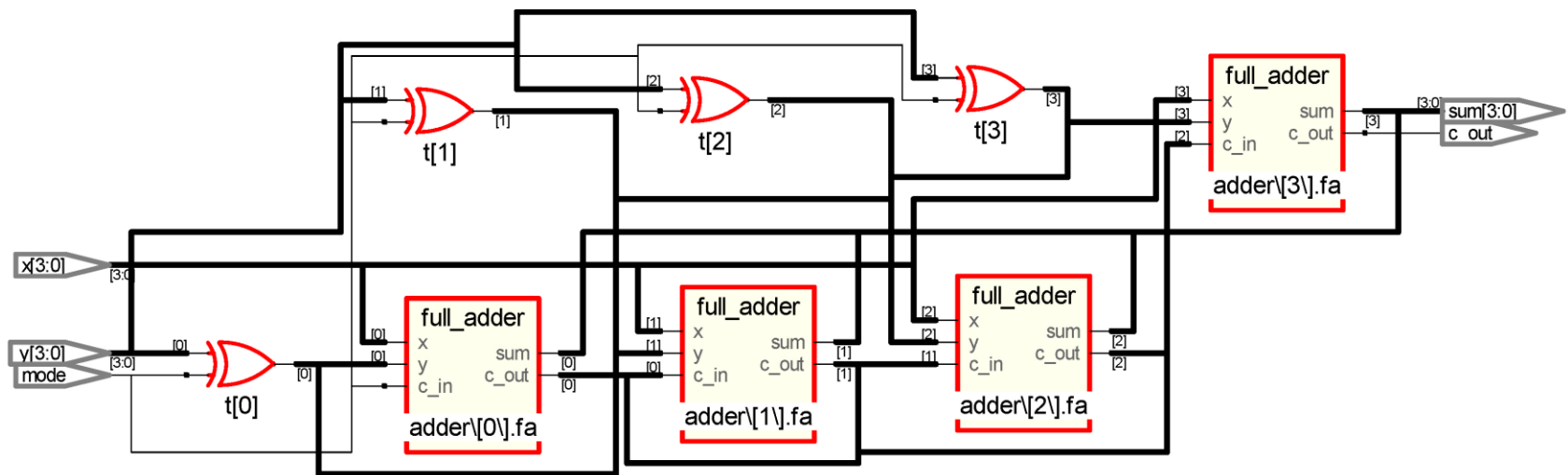

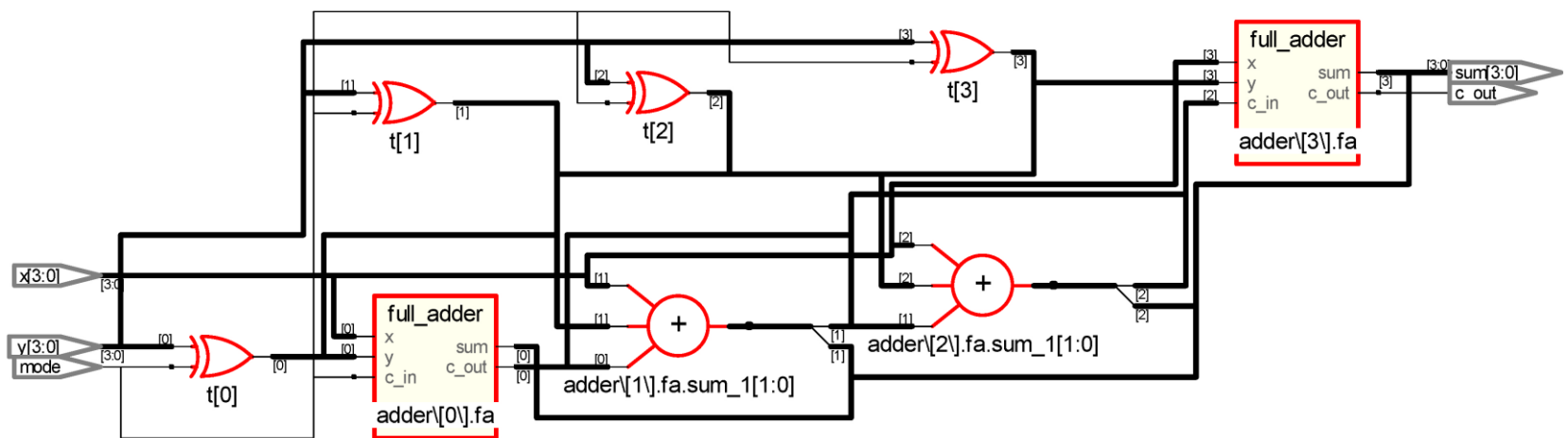(a) The RTL schematic

A Two's Complement Adder

❖ After dissolving the second and the third bits



(b) After dissolving the second and the third full adder modules

Syllabus

- ❖ Objectives
- ❖ Module
- ❖ Generate statements
 - Generate-loop statements
 - Generate-conditional statements
 - Generate-case statements

The generate Case Construct

```
generate for (i = 0; i < N; i = i + 1) begin: adder
    case (i)
        0: assign {c[i], sum[i]} = x[i] + y[i] + c_in;
        N-1: assign {c_out, sum[i]} = x[i] + y[i] + c[i-1];
        default: assign {c[i], sum[i]} = x[i] + y[i] + c[i-1];
    endcase
end endgenerate
```

A UDP Example

```
// an example of sequential UDP instantiations
parameter N = 4;
input  clk, clear;
output [N-1:0] qout;
....
genvar i;
generate for (i = 0; i < N; i = i + 1) begin: ripple_counter
    if (i == 0) // specify LSB
        T_FF tff (qout[i], clk, clear);
    else      // specify the rest bits
        T_FF tff (qout[i], qout[i-1], clear);
end endgenerate
```