

# Chapter 9: Processor Design Examples

# Syllabus

- Objectives
- Bus
- Data transfer
- General-purpose input and output
- Timers
- Universal asynchronous receiver and transmitter
- A simple CPU design

# Syllabus


- Objectives
- Bus
  - A  $\mu$ p system architecture
  - Bus structures
  - Bus arbitration
- Data transfer
- General-purpose input and output
- Timers
- Universal asynchronous receiver and transmitter
- A simple CPU design

# A Basic $\mu$ P System





**32-bit  $\mu$ P**

**16M SRAM**

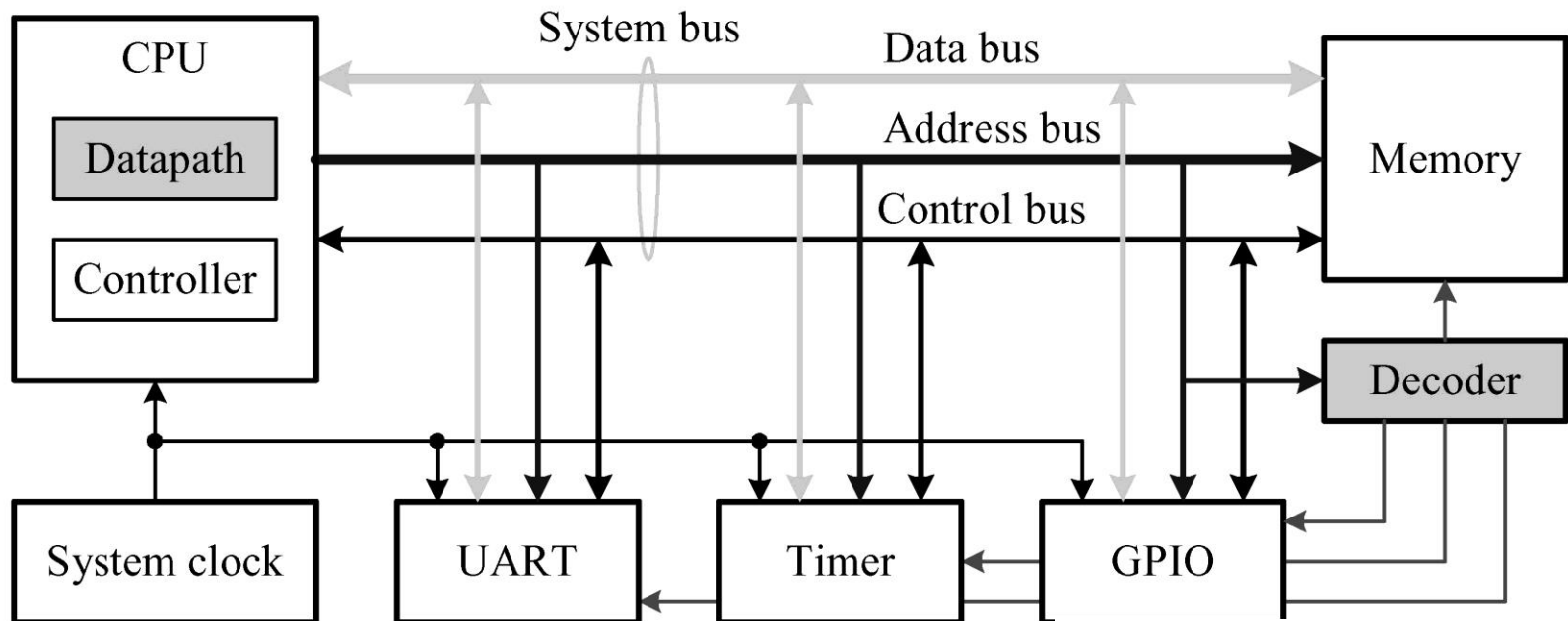

**Clock Gen  
& Timer**

  

**ESP8266:**

**Add More  
GPIOs  
With MCP23008**



# Syllabus

- Objectives
- Bus
  - A  $\mu$ p system architecture
  - Bus structures
  - Bus arbitration
- Data transfer
- General-purpose input and output
- Timers
- Universal asynchronous receiver and transmitter
- A simple CPU design

# Bus Structures

- Tristate bus
  - using tristate buffers
  - often called bus for short
- Multiplexer-based bus
  - using multiplexers

# A Tristate Bus

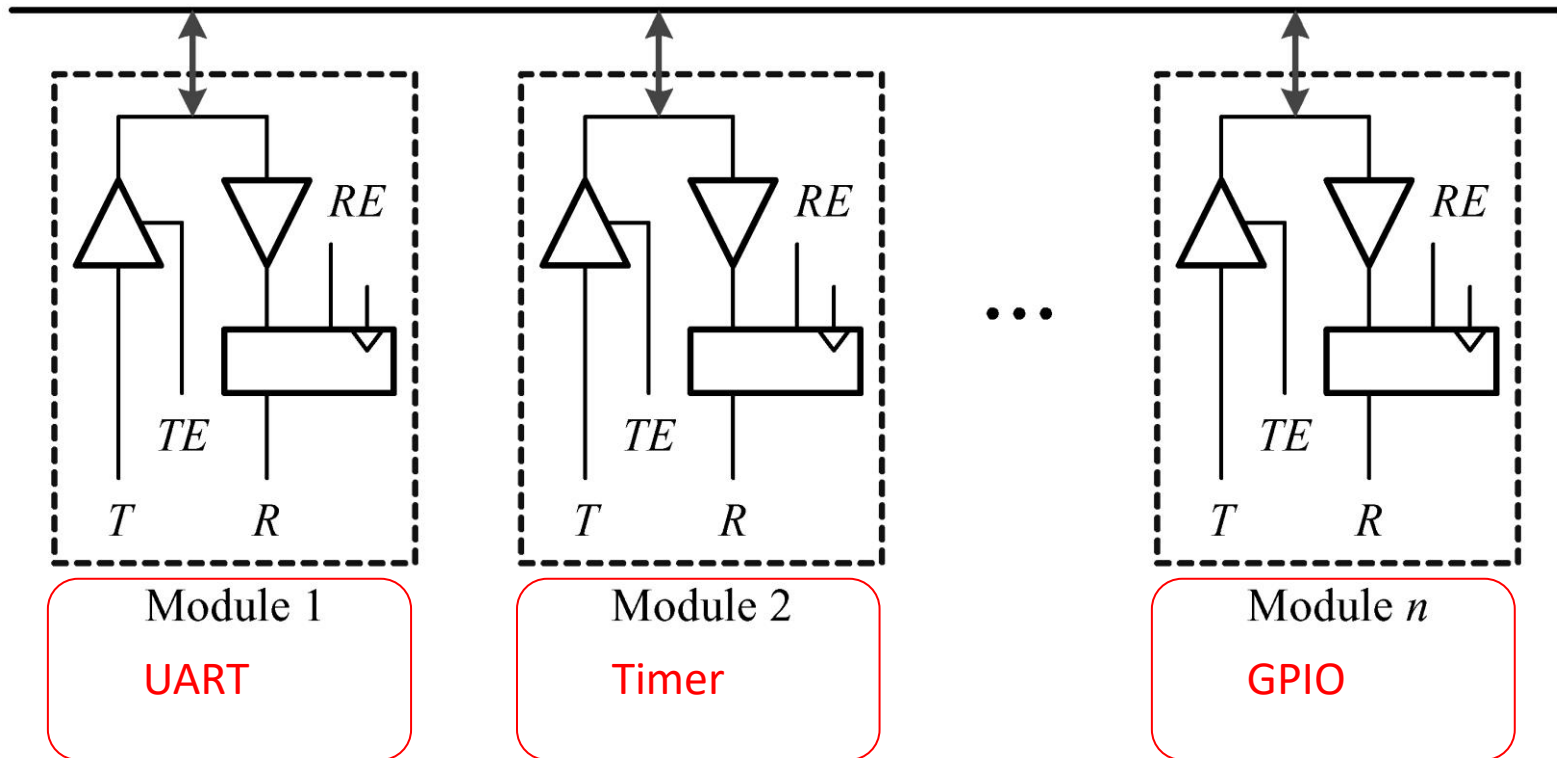 


# A Tristate Bus Example

// a tristate bus example

```
module tristate_bus (data, enable, qout);  
parameter N = 2; // define bus width  
input  enable;  
input  [N-1:0] data;  
output [N-1:0] qout;  
wire  [N-1:0] qout;
```


// the body of tristate bus
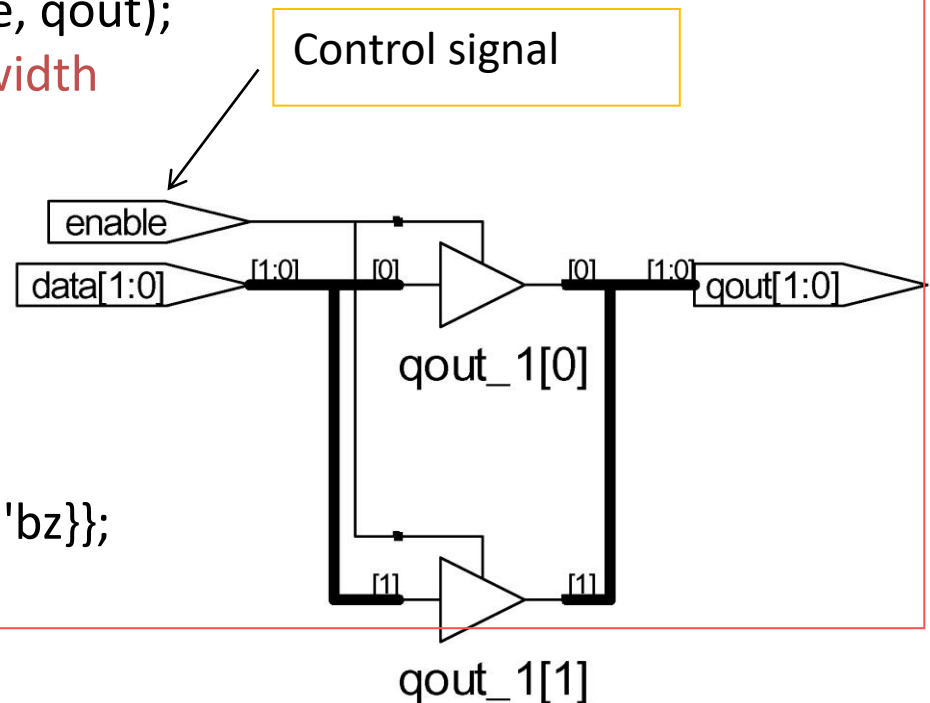
```
assign qout = enable ? data : {N{1'bz}};  
endmodule
```





# A Bidirectional Bus Example

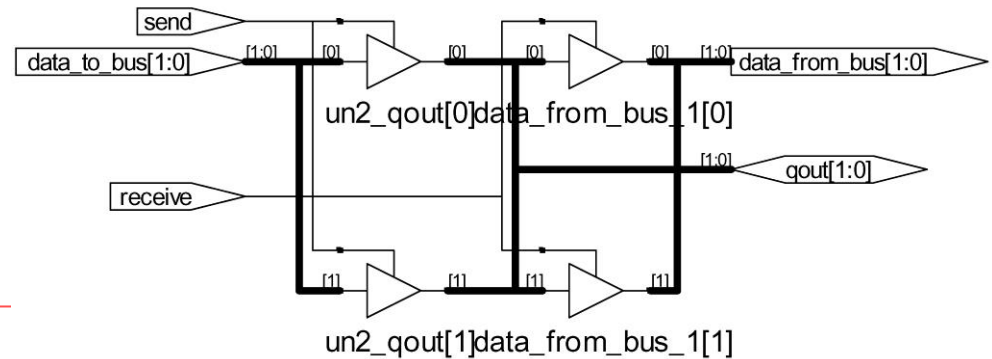

// a bidirectional bus example

```
module bidirectional_bus (data_to_bus, send, receive, data_from_bus,
qout);
```

```
parameter N = 2;           // define bus width
```

```
input  send, receive;
```

```
input  [N-1:0] data_to_bus;
```

```
output [N-1:0] data_from_bus;
```

```
inout  [N-1:0] qout;        // bidirectional bus
```

```
wire   [N-1:0] qout, data_from_bus;
```


// the body of tristate bus

```
assign data_from_bus = receive ? qout : {N{1'bz}};
```

```
assign          qout = send ? data_to_bus : {N{1'bz}};
```

```
endmodule
```

# A Multiplexer-Based Bus


 


# Syllabus


- Objectives
- Bus
  - A  $\mu$ p system architecture
  - Bus structures
  - Bus arbitration
- Data transfer
- General-purpose input and output
- Timers
- Universal asynchronous receiver and transmitter
- A simple CPU design
  
# Daisy-Chain Arbitration

- Types of bus arbitration schemes
  - daisy-chain arbitration
  - radial arbitration




(a) Daisy-chain arbitration

 


(b) Radial arbitration

# Homework 4

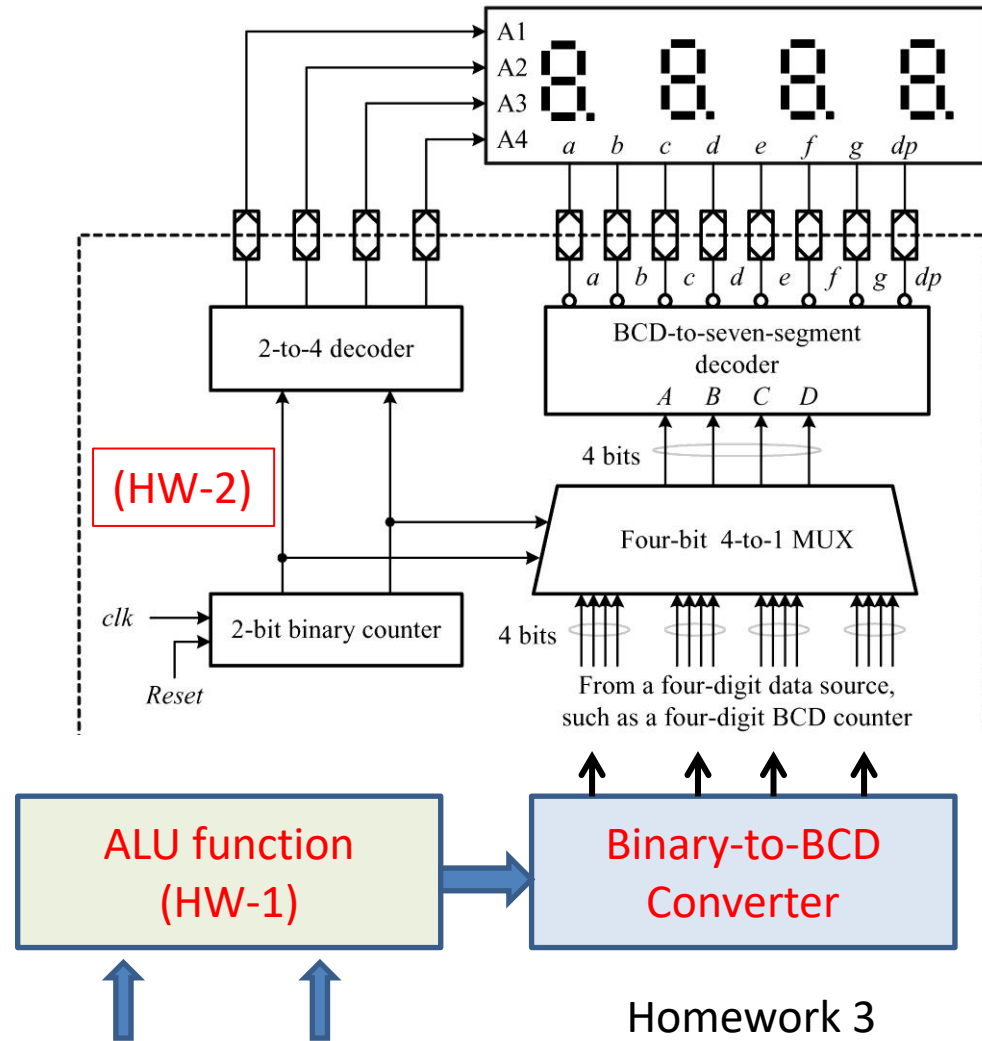


$X, Y = 0 \sim 2^{15}-1(B) = 0000 \sim 7FFF(H)$

# *uP for Homework Design*

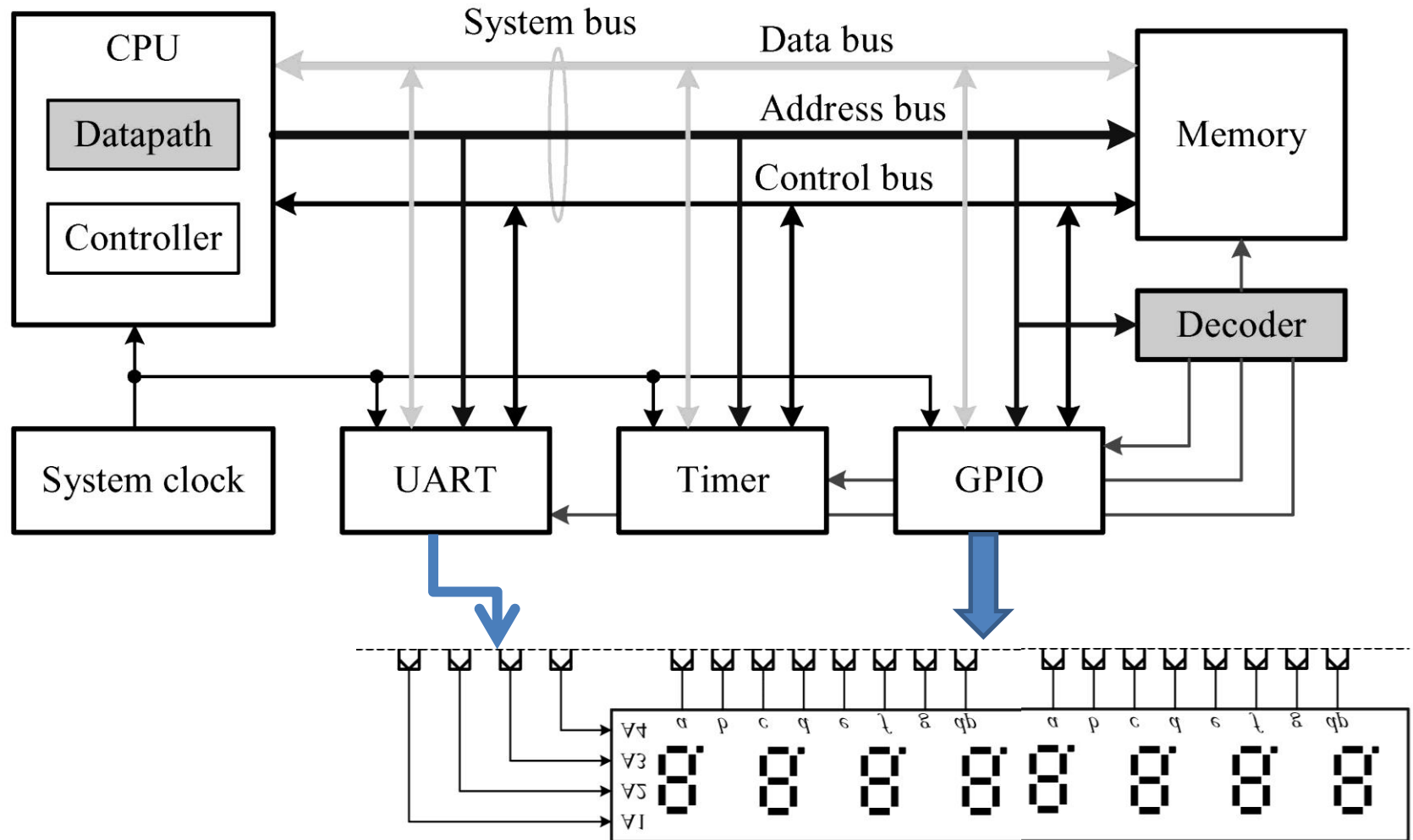

# *uP for Computer Design*

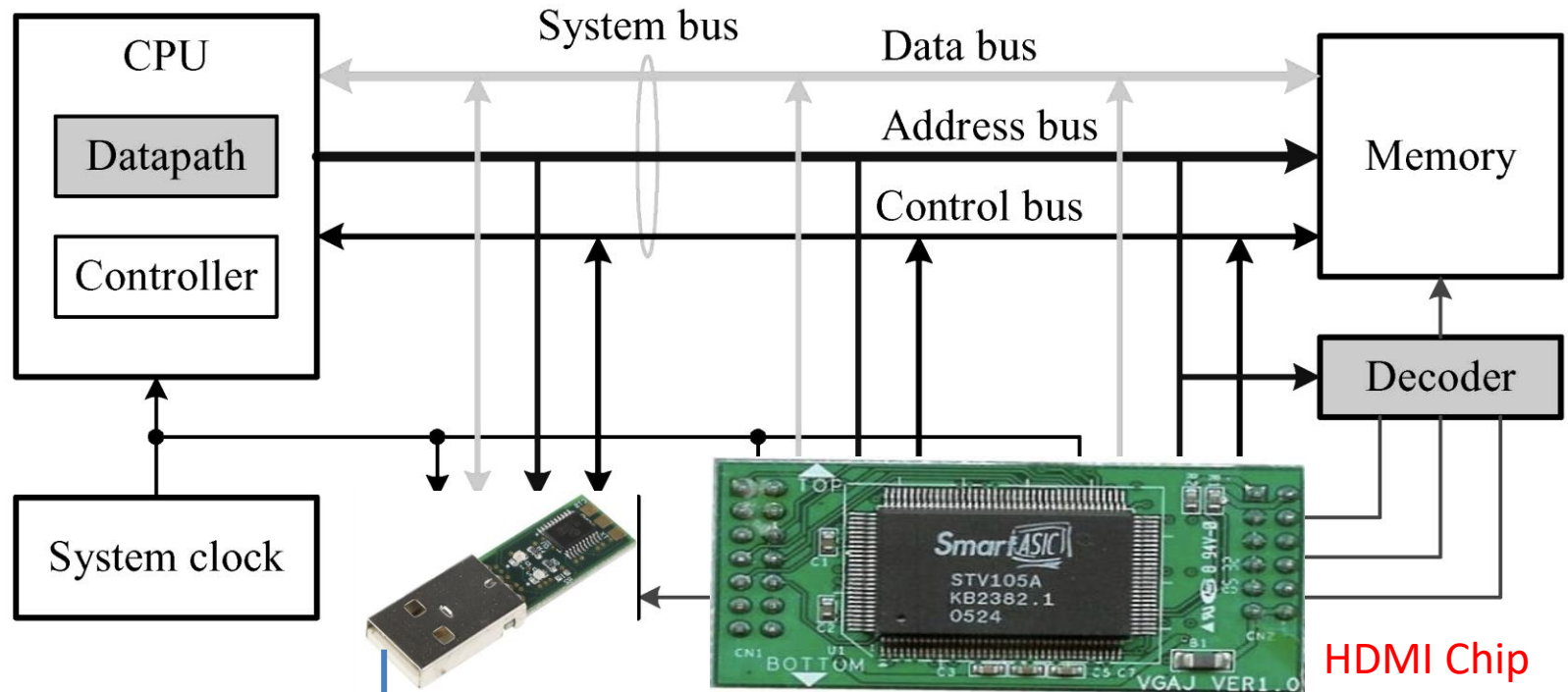

USB Chip



HDMI Chip



# Reference Design Examples

## **Basic Verilog Examples**

[https://web.csulb.edu/~rallison/Verilog\\_Examples\\_Table.htm](https://web.csulb.edu/~rallison/Verilog_Examples_Table.htm)

## **Useful verilog examples**

[http://jupiter.math.nctu.edu.tw/~weng/courses/IC\\_2007/PROJECT\\_MATH\\_CLASS1/3\\_DESIGN\\_COMPLEXITY/Verilog%20examples%20useful%20for%20FPGA%20&%20ASIC.htm](http://jupiter.math.nctu.edu.tw/~weng/courses/IC_2007/PROJECT_MATH_CLASS1/3_DESIGN_COMPLEXITY/Verilog%20examples%20useful%20for%20FPGA%20&%20ASIC.htm)

## **Design company**

[https://www.doulos.com/knowhow/verilog\\_designers\\_guide/](https://www.doulos.com/knowhow/verilog_designers_guide/)

## **Design Examples**

<https://verilogguide.readthedocs.io/en/latest/verilog/designs.html>


## **UART, Serial Port, RS-232 Interface**

<https://www.nandland.com/vhdl/modules/module-uart-serial-port-rs232.html>



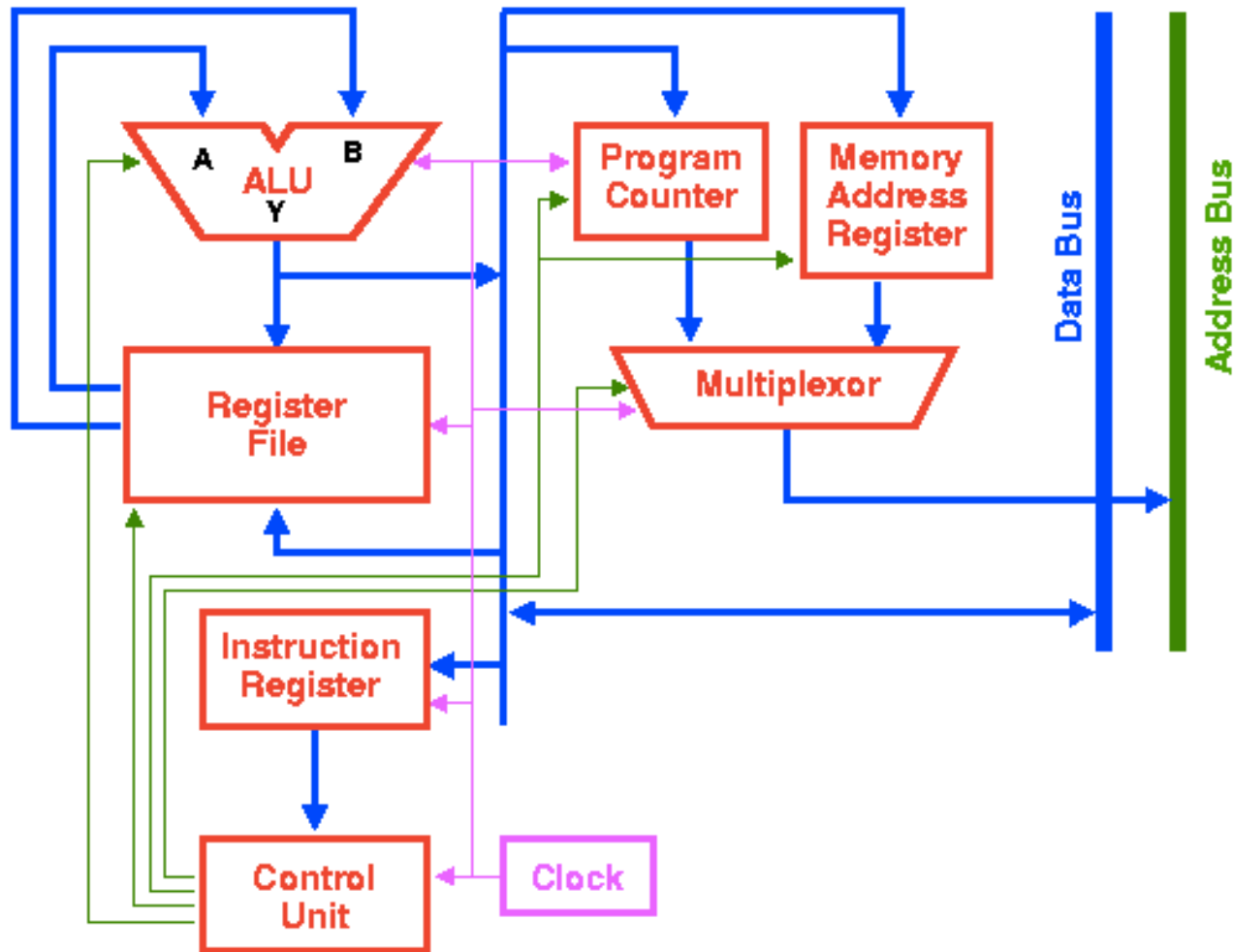
# 8-Bit RISC Processor I

<https://linus5.blogspot.com/2016/07/risc-processor.html>



# 8-Bit RISC Processor II

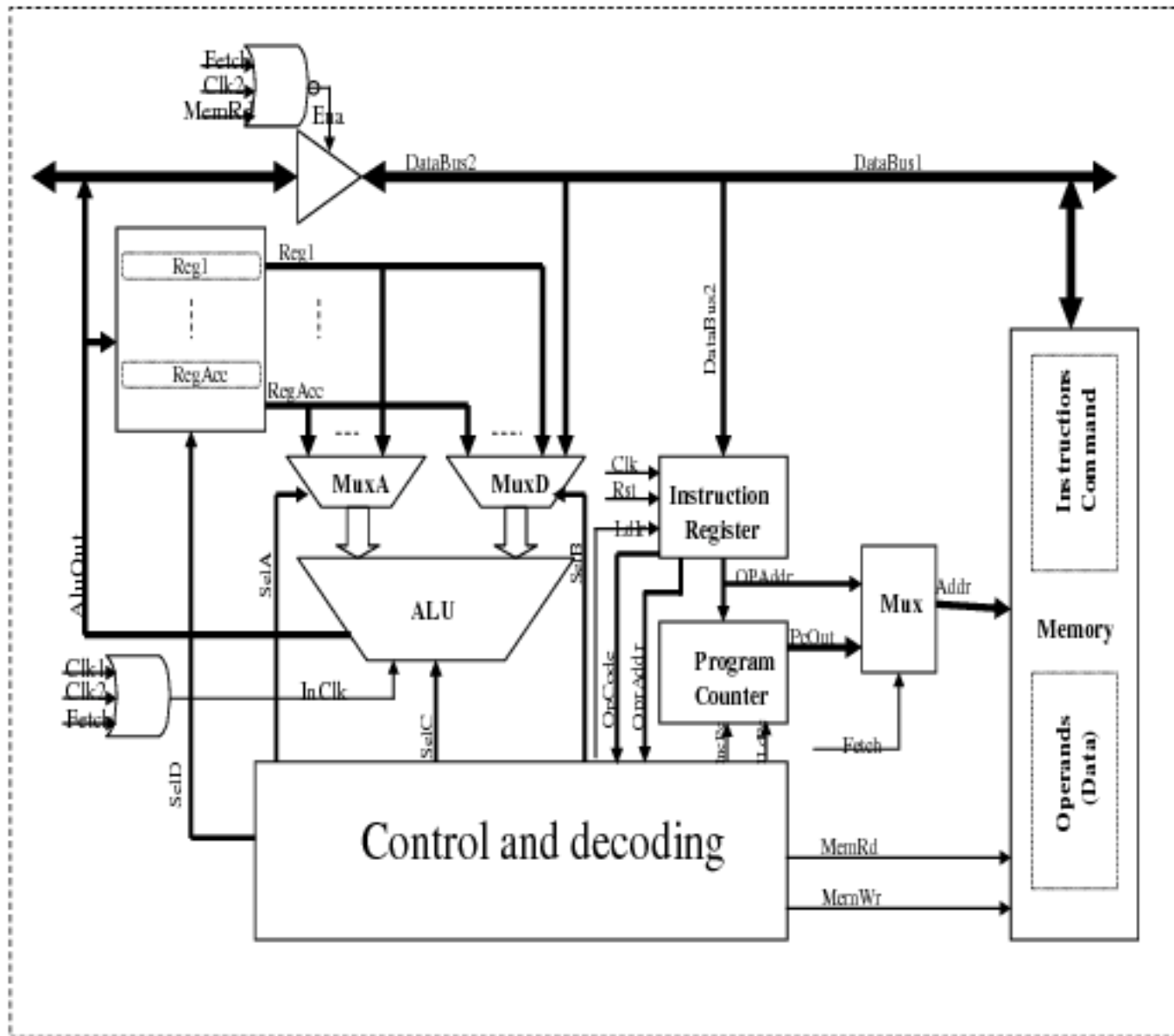

# 8-Bit RISC Processor III

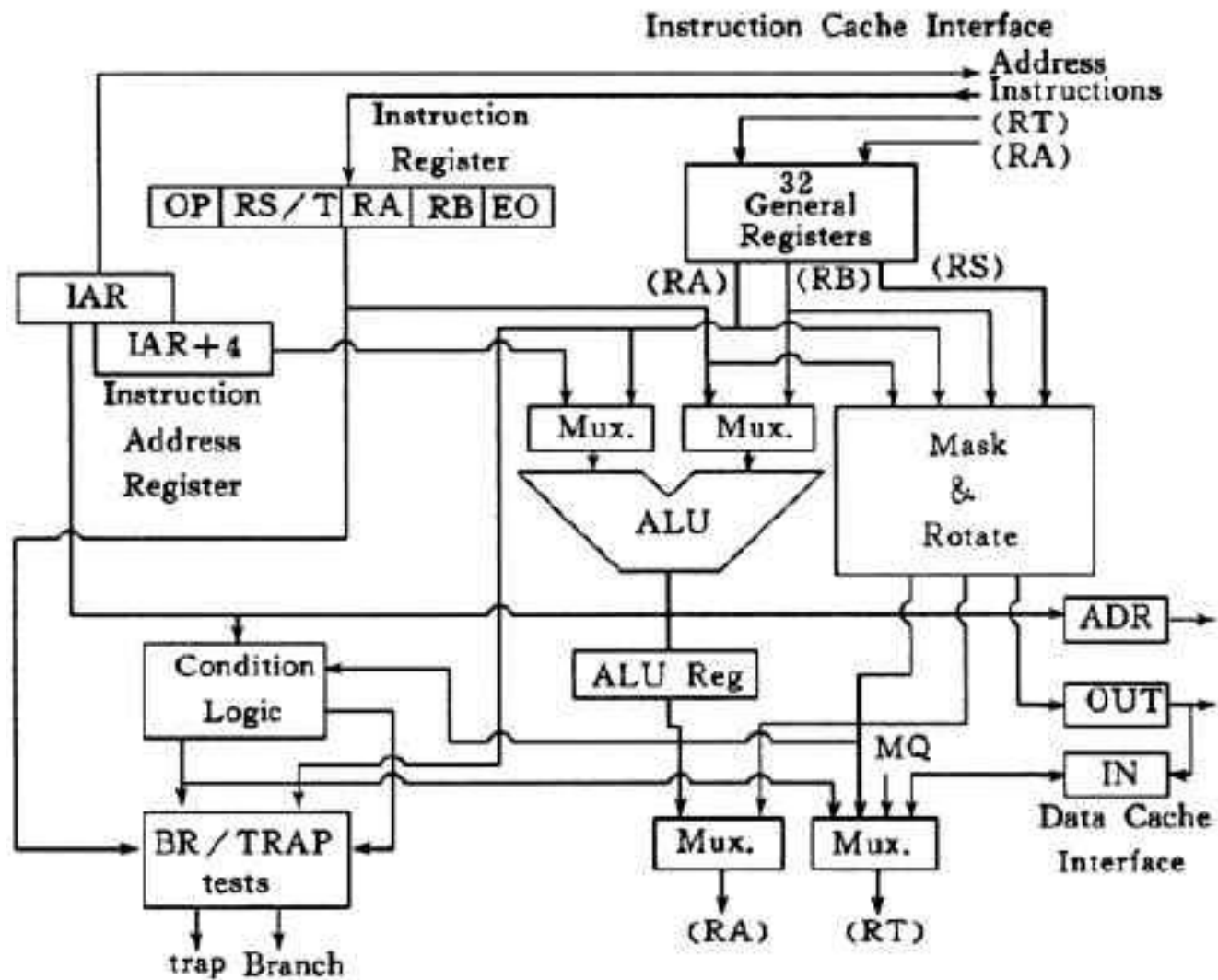


Fig. 3-2 IBM 801 Architecture

# 8-bit RISC CPU in Verilog

- <https://electronicstopper.blogspot.com/2017/06/8-bit-risc-cpu-in-verilog.html>

The Advantages of RISC will be discussed from a number of points of view

1. VLSI realization.
2. Computing speed.
3. Design cost and reliability.
4. HLL support.

THIS WEBSITE DOES NOT WORK PROPERLY WITH AD-BLOCK, CONSIDER WHITELISTING THIS WEBSITE IN AD-BLOCK

Editorial

VLSI

Arduino

Raspberry Pi

Circuits

Programming

Security

English

Book Summary

About Me

網站畫面

## 8 bit RISC CPU in Verilog

June 20, 2017



You can download all my project files for this project [HERE](#)



下載CPU之Verilog程式

### 1. INTRODUCTION

#### 1.1 RISC PROCESSORS

## RISC\_CPU

按名稱排序



\_ngo



\_xmsgs



accum\_summary.html



accum.v



alu.v



clkgen.v



decoder.v









instreg.v




iobuffer.v



iseconfig

      

# 8-bit RISC CPU Architecture

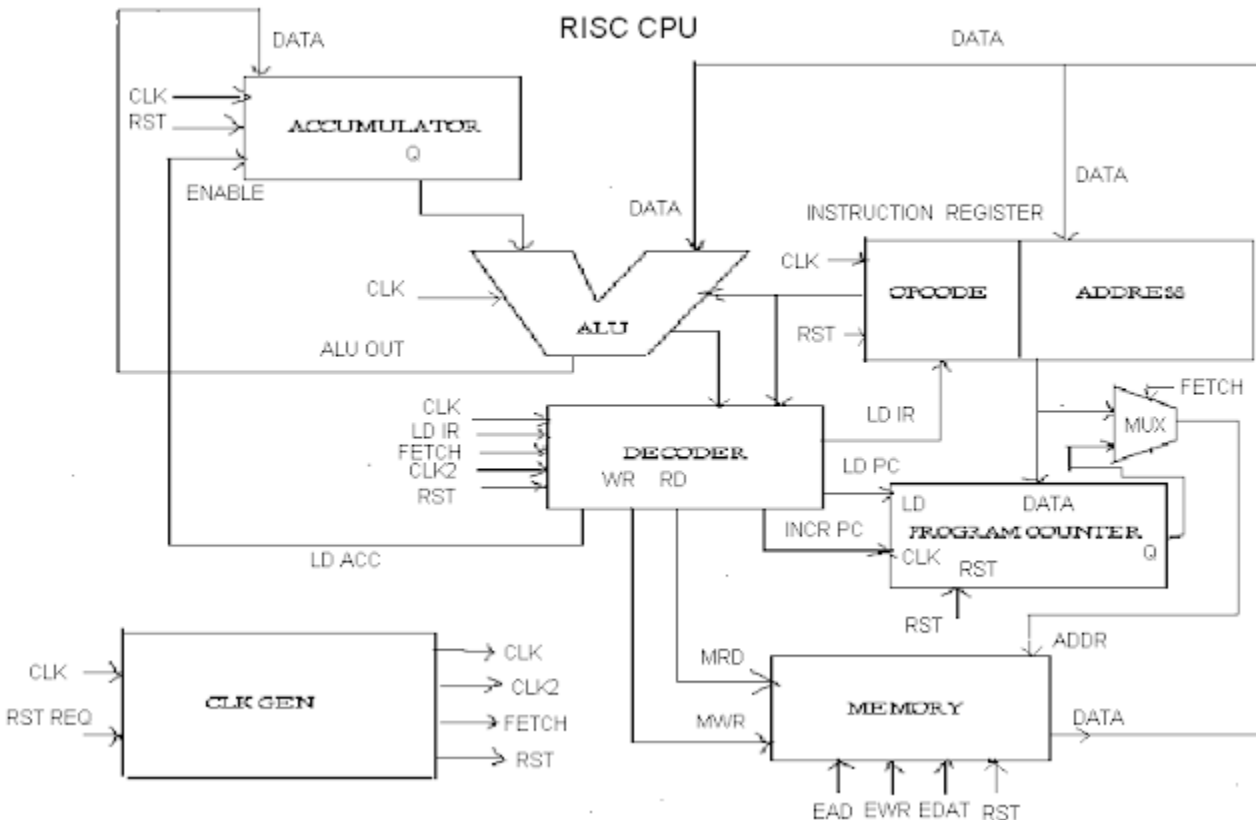

Top level module:

1. Clock Generator
2. Memory
3. Multiplexer
4. Program Counter
5. Instruction Register
6. Accumulator
7. Arithmetic and Logic Unit
8. Decoder
9. IO Buffer


Homework 5: 驗證9個module functions → 設計9個stimulus code  
Homework 6: 修改testbench.v之測試資料



The major characteristics of a RISC processor are

1. Relatively **few instructions**.
2. Relatively **few addressing modes**.
3. Memory access limited to **load and store instructions**.
4. All operations **done within the registers** of the CPU.
5. **Fixed –length**, easily decoded instruction format.
6. **Single –cycle** instruction execution.

# Architecture of 8-Bit RISC CPU

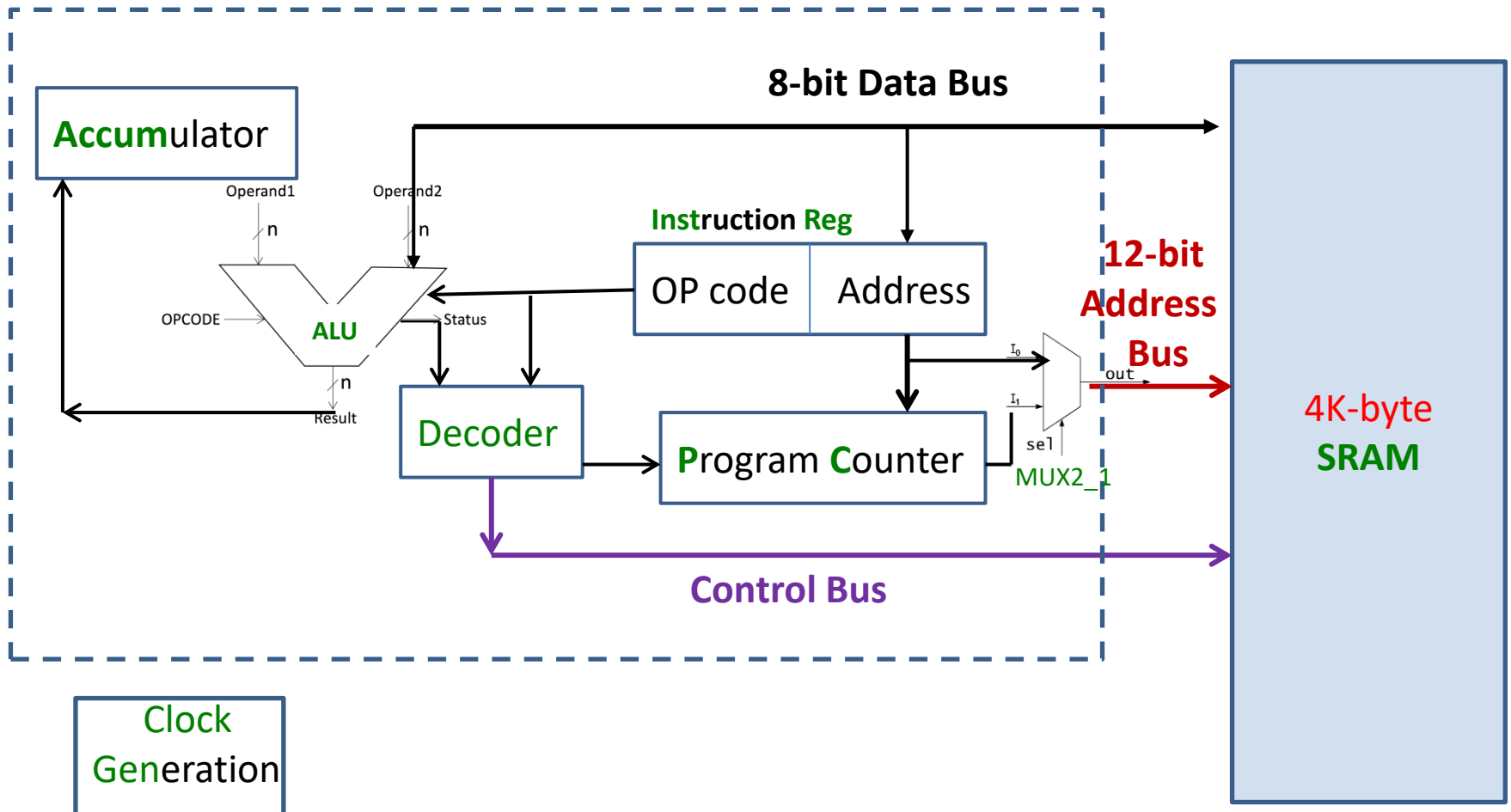


```
module topmodule(clk,rstreq,ewr,ead,edat,zr);
```

```
input clk, rstreq, ewr;           input [4:0] ead;  
input [7:0] edat;                output zr;           wire zr;   wire ldac, ldir;  
wire clk1, clk2, fch, rst;       wire [7:0] alu_out, acc_out; wire [7:0] mdat;  
wire [4:0] adir, adpc, admem; wire [2:0] opcd;   wire ldpc, pclk, aclk, mrd, mwr;
```

```
iobuffer io1( .clk2(clk2), .mrd(mrd) , .fch(fch), .alu_out(alu_out), .mdat(mdat));  
accum accum1( .clk(clk1), .rst(rst), .alu_out(alu_out), .ldac(ldac) , .acc_out(acc_out));  
clkgen clkgen1( .clk(clk), .rstreq(rstreq), .clk1(clk1), .clk2(clk2), .fch(fch), .rst(rst));  
decode decoder1( .clk1(clk1), .clk2(clk2), .fch(fch), .rst(rst), .opcd(opcd), .ldir(ldir),  
                .ldir(ldir),.ldac(ldac),.mrd(mrd),.mwr(mwr),.ldpc(ldpc),.pclk(pclk),.aclk(aclk));  
instreg instreg1( .clk(clk1) , .rst(rst), .ldir(ldir), .mdat(mdat), .adir(adir), .opcd(opcd));  
alu alu1( .aclk(aclk) , .mdat(mdat) , .acc_out(acc_out) , .opcd(opcd) ,  
          .alu_out(alu_out) , .zr(zr) );  
memory mem1(.rst(rst) , .mrd(mrd) , .mwr(mwr) , .ewr(ewr), .mad(admem),  
            .ead(ead), .edat(edat), .mdat(mdat));  
pc pc1( .pclk(pclk), .rst(rst), .adir(adir), .ldpc(ldpc), .adpc(adpc));  
mux2_1 mux2( .adir(adir), .adpc(adpc), .fch(fch) , .admem(admem));  
endmodule
```

# Architecture of 8-Bit RISC CPU


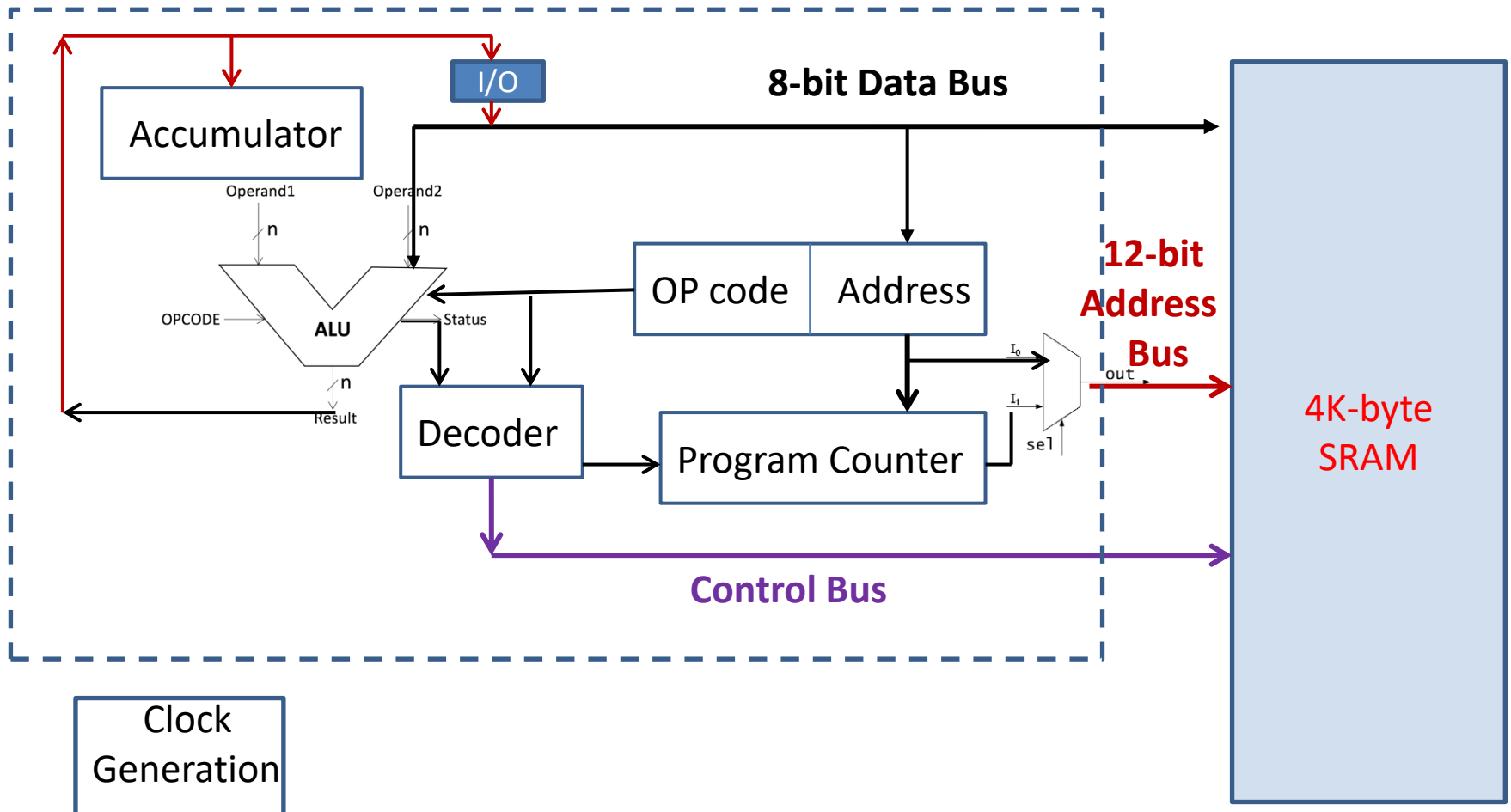

  
# CLOCK GENERATOR Module





For every negative edge of clock, clock2 is generated

For every positive edge of clock2, fetch signal is generated.



# Clock Gnerator → Decoder

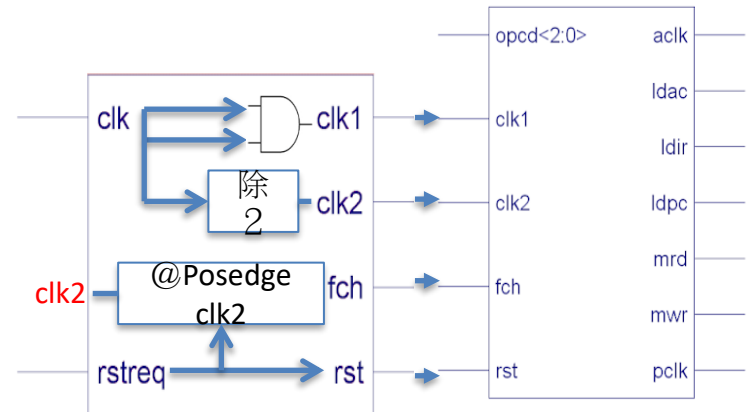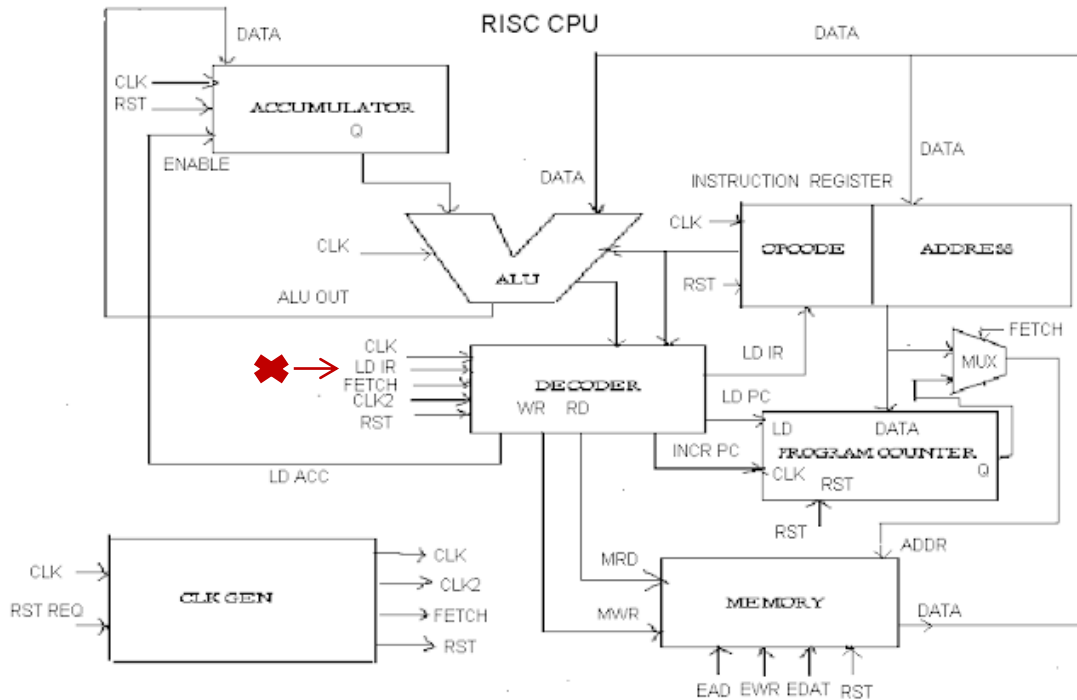

Clock Generator

Decoder

```
module clkgen(clk,rstreq,clk1,clk2,fch,rst);
```

## CODE FOR CLOCK GENERATOR

```
module clkgen(clk,rstreq,clk1,clk2,fch,rst);
```

```
input clk,rstreq;
```

```
output clk1,clk2,fch,rst;
```

```
wire c1; reg c2,c3; reg rst;
```

```
assign c1 = clk && clk; // and delay for synchronous
```

```
assign clk1 = c1;
```

```
always @(negedge c1 or negedge rstreq) begin
```

```
if (!rstreq) begin c2 <= 0; rst<=1; end else begin c2 <= ~c2; clk2 <= c2 ; end
```

```
always @(posedge c2 or negedge rstreq) begin
```


```
if (!rstreq) c3<= 0 else begin c3<= ~ c3; fch<= c3 ; end
```

```
end
```

```
Endmodule
```

//網站沒有



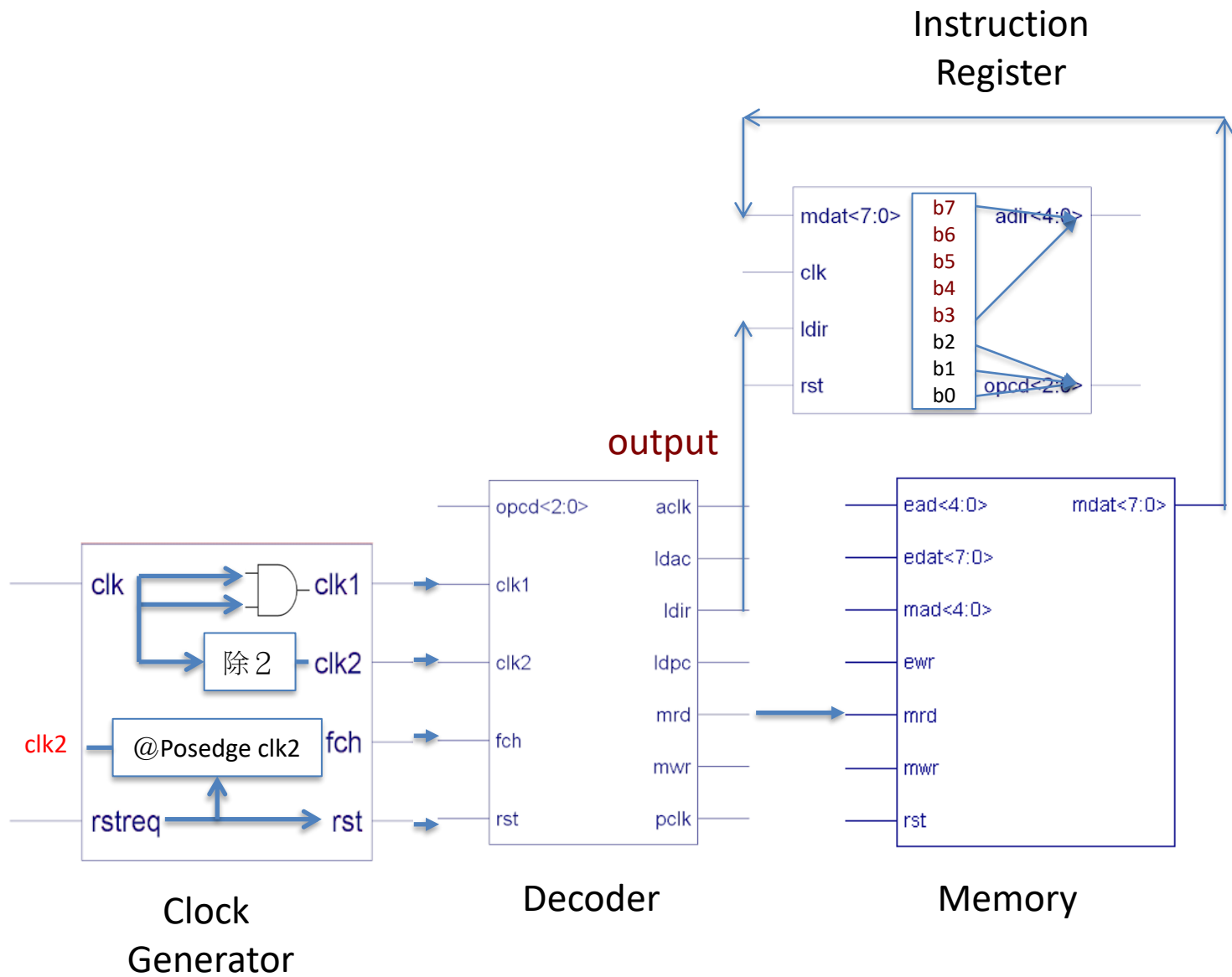



CPU工作劇本:

CPU2讀取  
SRAM指令

CPU2解碼  
指令與執行

CPU儲存  
結果

011 111



clk


clk2

fch

rstreq

Decoder Operation

Read data from memory

 

assign ldir = dout[0];

assign mrd = dout[1];

assign mwr = dout[2];

assign ldpc = dout[3];

assign ldac = dout[4];

assign pclk = dout[5];

3'b100 : aclk = 0;

default : aclk = 1;

## Code or Decoder

```
module decode(clk1,clk2,fch,rst,opcd,ldir,ldac,mrd,mwr,ldpc,pclk,aclk);
```

```
input clk1, clk2, rst, fch;
```

```
output ldir, ldac, mrd, mwr, ldpc, pclk, aclk;
```

```
reg aclk;
```

```
wire [2:0] seq;
```

```
input [2:0] opcd;
```

```
reg [7:0] dout;
```

```
assign seq = {clk1,clk2,fch};
```

```
always @(*) begin
```

```
  if(!rst) dout = 0; else begin
```

```
    case(seq) 3'b011 : dout = 6'b000000;
```

```
             3'b111 : dout = 6'b000010;
```

```
             3'b001 : dout = 6'b000011;
```

```
             3'b101 : dout = 6'b000011;
```

```
             3'b010 : dout = 6'b000000;
```

```
             3'b110 : begin
```

Read instruction from memory  
to instruction register

Decoding opcode from  
instruction register


```
              case(opcd) 3'b010 : dout = 6'b100010;
```

```
                    3'b011 : dout = 6'b100010;
```

```
                    3'b100 : dout = 6'b100010;
```

```
                    3'b101 : dout = 6'b100010;
```
 
```
                    default: dout = 6'b100000; endcase end
```




# Memory Module

```
module memory(rst,mrd,mwr,ewr,mad,ead,edat,mdat);
```

```
input rst, mrd, mwr, ewr;           input [4:0] mad, ead;           input [7:0] edat,  
inout [7:0] mdat;           reg [7:0] memr [31:0] ;           reg [7:0] temp;  
    // edata: external data,  mdata: CPU-memory data
```

```
always @(*) if (!rst) begin  
    if (!rst) begin if(ewr == 1) begin memr[ead] <= edat; end end  
    else begin if(mwr == 1) begin memr[mad] <= mdat; end  
        else if (mrd == 1) begin temp <= memr[mad]; end  
        else begin temp <= 'bzzzzzzzz; end  
    end  
end
```

```
assign mdat = temp;  
endmodule
```

 

# Instruction Register Module

```
module instreg(clk,rst,ldir,mdat,adir,opcd);
```

```
input clk, ldir, rst;
```

```
output [4:0] adir;
```

```
reg [4:0] adir;
```

```
input [7:0] mdat;
```

```
output [2:0] opcd;
```

```
reg [2:0] opcd;
```


```
always @(posedge clk or negedge rst) begin
```


```
    if (!rst) begin opcd <= 0; adir <= 0; end
```


```
    else if (ldir == 1) begin opcd <= mdat[7:3] ; adir <= mdat[2:0] ; end
```

```
end
```



```
endmodule
```

 

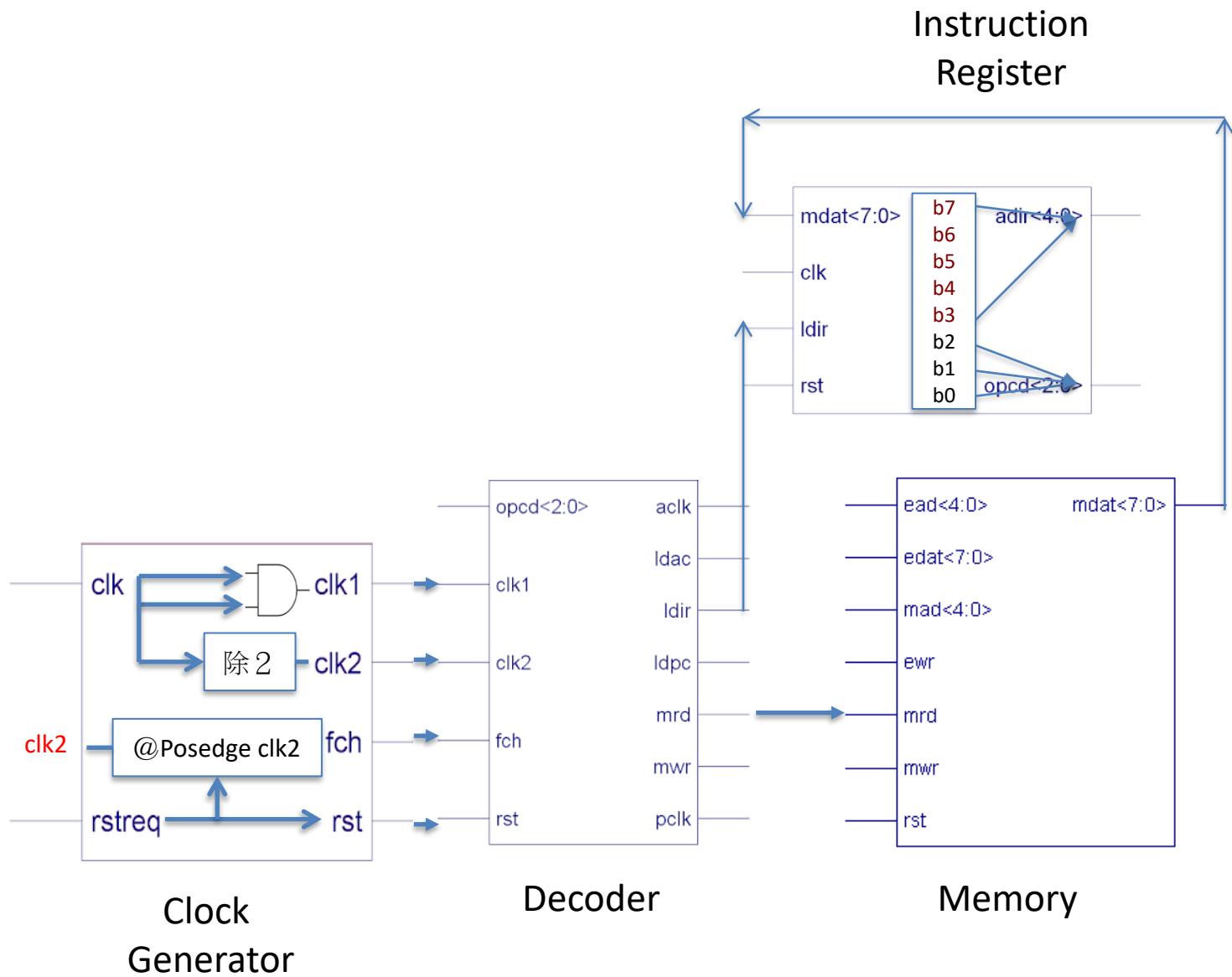

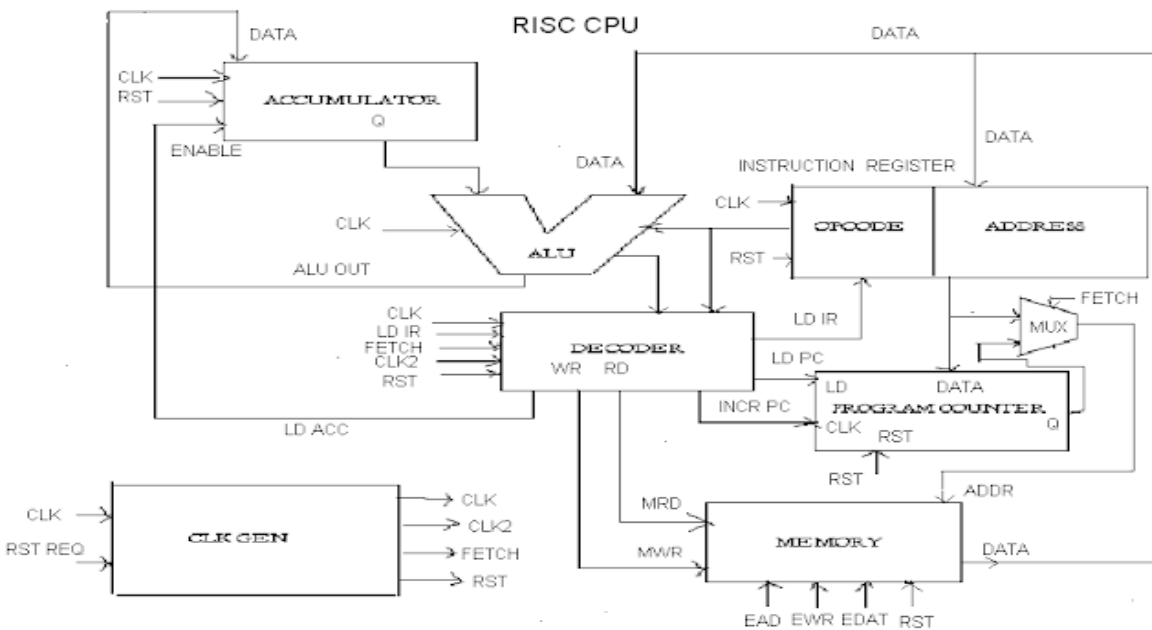


## Instruction Register

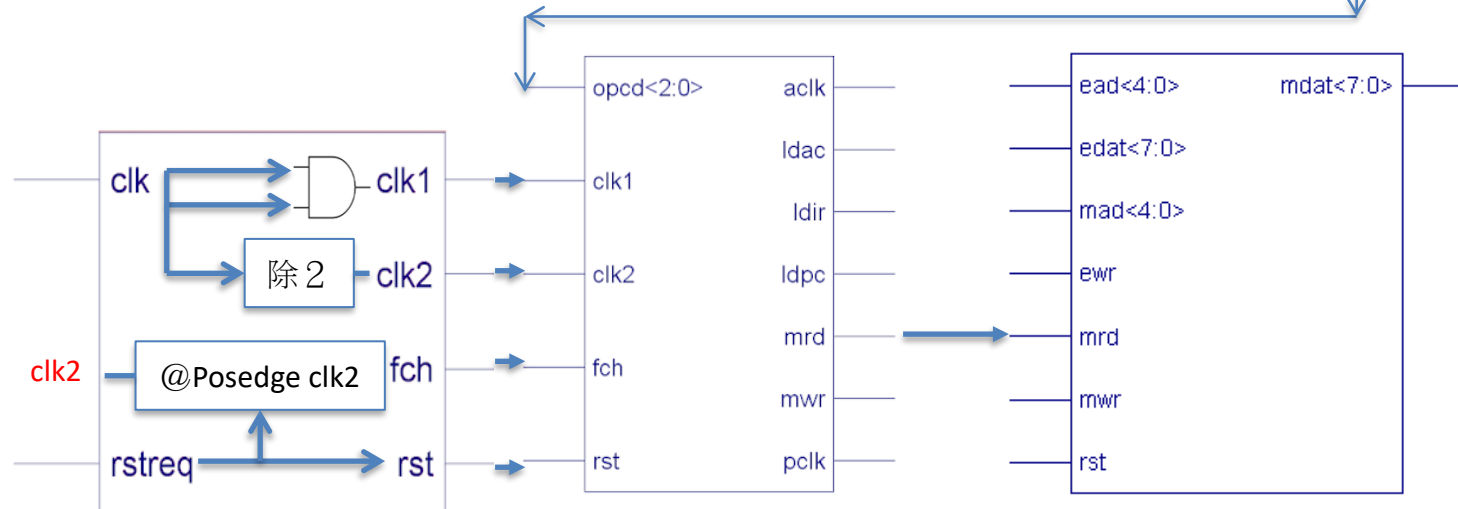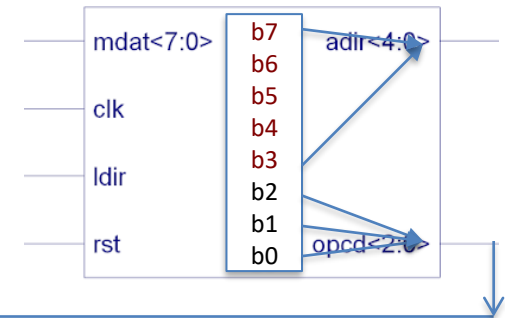

## Clock Generator


## Decoder

## Memory

 

## Decoder Operation

Read data from memory

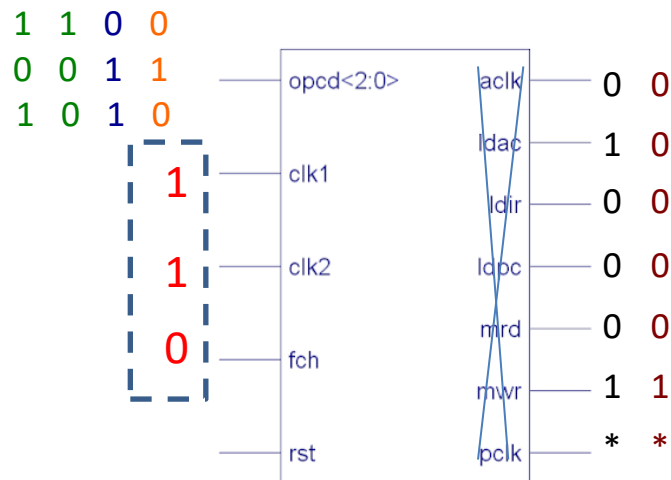

← `assign ldir = dout[0];`  
 ← `assign mrd = dout[1];`  
`assign mwr = dout[2];`  
`assign ldpc = dout[3];`  
`assign ldac = dout[4];`  
`assign pclk = dout[5];`

`3'b100 : aclk = 0;`  
`default : aclk = 1;`

**default:** `dout = 6'b100000;`    `3'b010 : dout = 6'b100010;`



## Cpde for Decoder

```
module decode(clk1,clk2,fch,rst,opcd,ldir,ldac,mrd,mwr,ldpc,pclk,aclk);
```

```
input clk1, clk2, rst, fch;
```

```
output ldir, ldac, mrd, mwr, ldpc, pclk, aclk;
```

```
reg aclk;
```

```
wire [2:0] seq;
```

```
input [2:0] opcd;
```

```
reg [7:0] dout;
```

```
assign seq = {clk1,clk2,fch};
```

```
always @(*) begin
```

```
  if(!rst) dout = 0; else begin
```

```
    case(seq) 3'b011 : dout = 6'b000000;
```

```
            3'b111 : dout = 6'b000010;
```

```
            3'b001 : dout = 6'b000011;
```

```
            3'b101 : dout = 6'b000011;
```

```
            3'b010 : dout = 6'b000000;
```

```
            3'b110 : begin
```

Read instruction from memory  
to instruction register

Decoding opcode from  
instruction register

```
      case(opcd) 3'b010 : dout = 6'b100010;
```

```
                3'b011 : dout = 6'b100010;
```

```
                3'b100 : dout = 6'b100010;
```

```
                3'b101 : dout = 6'b100010;
```

```
                default: dout = 6'b100000; endcase end
```


## OPCODE for Decoder

### Instruction Opcode

|              |     |  |
|--------------|-----|--|
| Halt         | 000 | //控制所有module電路皆Halt                        |
| Skip of zero | 001 | //跳到0結果                                    |
| Add          | 010 | // Adder operation by controlling ALU      |
| And          | 011 | // And operation by controlling ALU        |
| Xor          | 100 | // Xor operation by controlling ALU        |
| Load         | 101 | // Load data by controlling Bus            |
| Store        | 110 | // Store data by controlling Bus           |
| Jump         | 111 | // Jump to 副程式 by changing Program Counter |

1 1 0 0  
0 0 1 1  
1 0 1 0

1  
1  
0

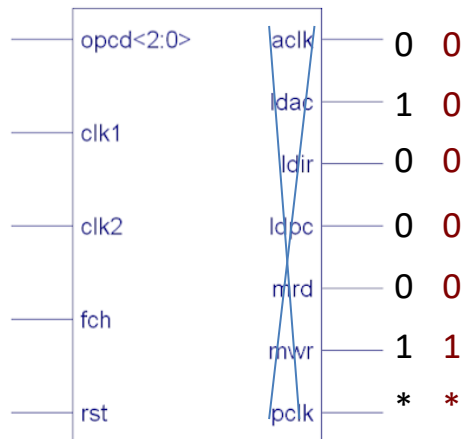

assign ldir = dout[0];

assign mrd = dout[1];

assign mwr = dout[2];



assign ldpc = dout[3];

assign ldac = dout[4];

assign pclk = dout[5];

//program counter之clock

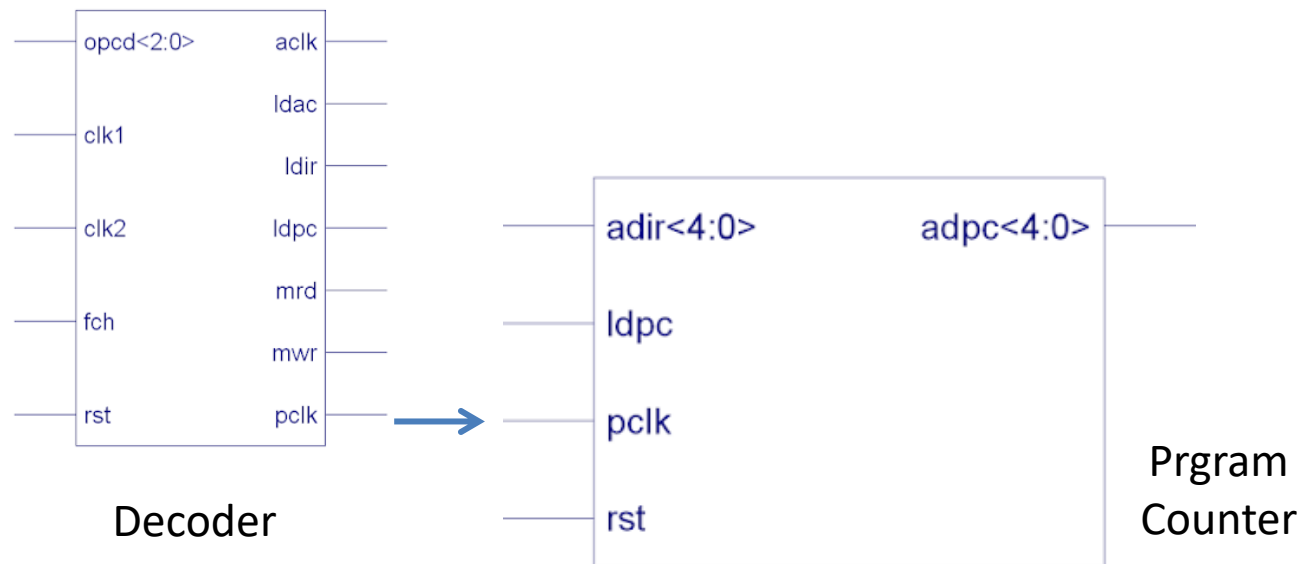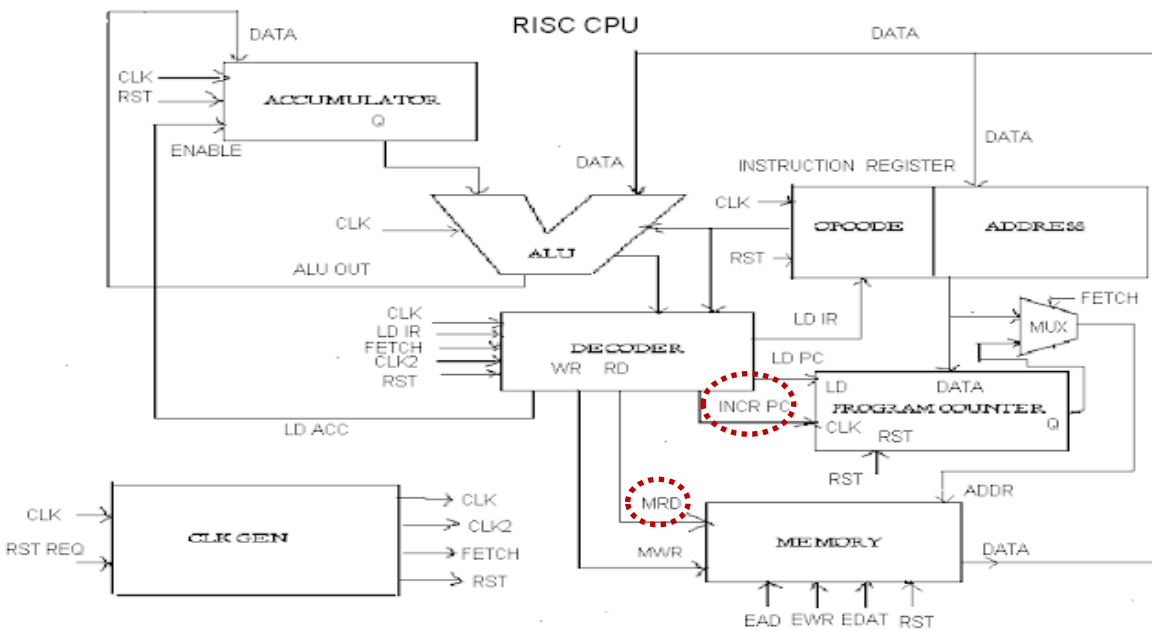
default: dout = 6'b100000; 3'b010 : dout = 6'b100010;


 
## Cpde for Program Counter


```
module pc( pclk, rst, adir, ldpc, adpc);  
  
input pclk, rst, ldpc;           input [4:0] adir;  
output [4:0] adpc;  
reg [4:0] temp1;  
  
    always @ (posedge pclk or negedge rst) begin  
        if (!rst) begin temp1 <= 0; end  
        else if ( ldpc == 1) begin temp1 <= adir; end  
        else begin temp1 <= temp1 + 1; end  
    end  
  
    assign adpc = temp1;  
  
endmodule
```





## Decoder Operation

Read data from memory

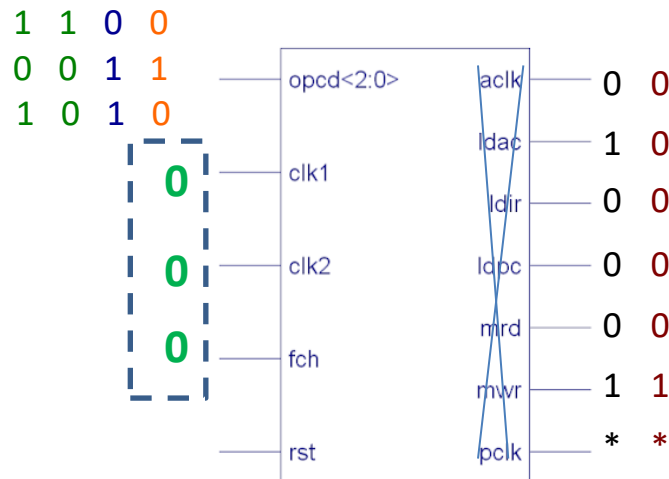

← assign **ldir** = dout[0];  
 ← assign **mrd** = dout[1];  
 assign **mwr** = dout[2];  
 assign **ldpc** = dout[3];  
 assign **ldac** = dout[4];  
 assign **pclk** = dout[5];

3'b100 : aclk = 0;  
 default : aclk = 1;

**default:** dout = 6'b100000;    3'b010 : dout = 6'b100010;

# Decoder module 2

```
3'b000 : begin case(opcd)
          3'b010 :      dout = 6'b010010;
          3'b011 : begin dout = 6'b010010; end
          3'b100 : begin dout = 6'b010010; end
          3'b101 : begin dout = 6'b010010; end
          3'b110 : begin dout = 6'b000100; end
          3'b001 : begin dout = 6'b100000; end
          3'b111 : begin dout = 6'b001000; end
          default : begin dout = 6'b000000; end endcase
```


## OPCODE for Decoder

### Instruction Opcode

|              |     |  |
|--------------|-----|--|
| Halt         | 000 | //控制所有module電路皆Halt                        |
| Skip of zero | 001 | //跳到0結果                                    |
| Add          | 010 | // Adder operation by controlling ALU      |
| And          | 011 | // And operation by controlling ALU        |
| Xor          | 100 | // Xor operation by controlling ALU        |
| Load         | 101 | // Load data by controlling Bus            |
| Store        | 110 | // Store data by controlling Bus           |
| Jump         | 111 | // Jump to 副程式 by changing Program Counter |

```

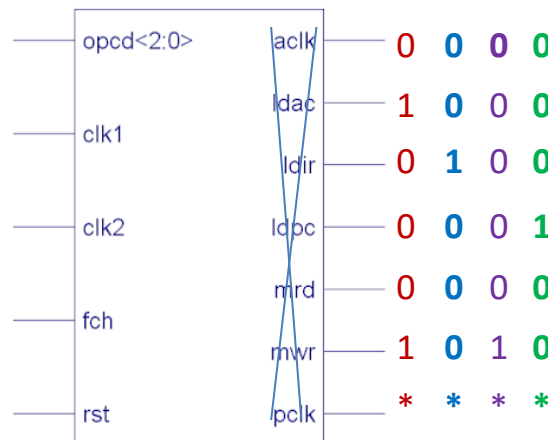1 0 1 1 1 0 0
1 0 1 0 0 1 1
1 1 0 1 0 1 0
  
```



```

assign ldir = dout[0];
assign mrd  = dout[1];
assign mwr  = dout[2];
Assign ldpc = dout[3];
assign ldac = dout[4];
assign pclk = dout[5];
  
```


//program counter之clock

```

default: dout = 6'b100000;  3'b010 : dout = 6'b100010;
  
```

## Decoder Output

1 0 1  
1 0 1  
1 1 0

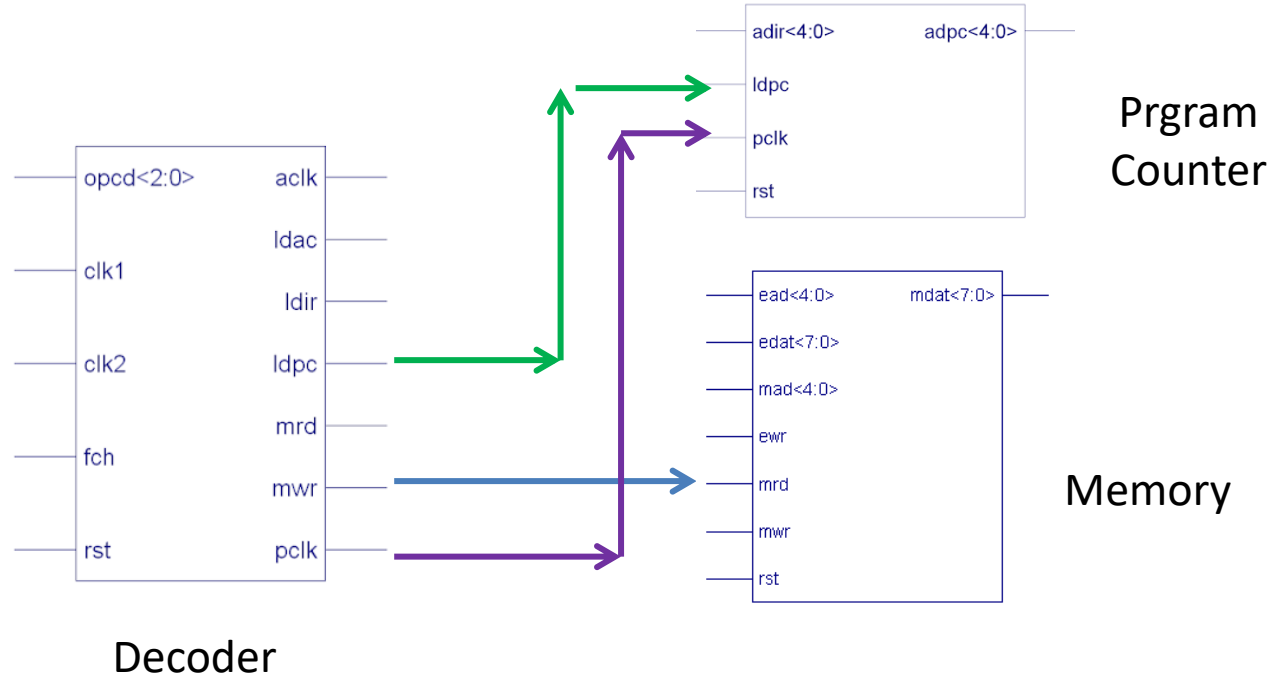



# Decoder module 3

```
3'b100 : begin case(opcd)  
    3'b010 :      dout = 6'b010010;  
    3'b011 : begin dout = 6'b010010; end  
    3'b100 : begin dout = 6'b010010; end  
    3'b101 : begin dout = 6'b010010; end  
    3'b001 : begin dout = 6'b100000; end  
    3'b111 : begin dout = 6'b101000; end  
    3'b110 : begin dout = 6'b000100; end  
    default : begin dout = 6'b000000; end endcase  
endcase end end  
  
assign ldir = dout[0];           assign mrd = dout[1];  
assign mwr = dout[2];           assign ldpc = dout[3];  
assign ldac = dout[4];          assign pclk = dout[5];
```

# Decoder module 4

```
always @(*) begin
    if(!rst) begin aclk = 0; end
    else begin
        case(seq) 3'b100 : aclk = 0;
                    default : aclk = 1; endcase
    end
end
endmodule
e
```

# ALU (Arithmetic Logic Unit) module 4

```
module alu (aclk,mdat,acc_out, opcd, alu_out, zr);
```

```
input aclk;           input [7:0] mdat, acc_out;
```

```
output [7:0] alu_out;
```

```
reg [7:0] a,alu_out;
```

```
input [2:0] opcd;
```

```
output zr;
```

```
wire zr;
```

```
always @ ( posedge aclk ) begin
```

```
    case (opcd) 3'b000 : begin a <= acc_out; end
```

```
                3'b001 : begin a <= acc_out; end
```

```
                3'b010 : begin a <= {mdat + acc_out}; end
```

```
                3'b011 : begin a <= {mdat & acc_out}; end
```

```
                3'b100 : begin a <= {mdat ^ acc_out}; end
```

```
                3'b101 : begin a <= mdat; end
```

```
                3'b110 : begin a <= acc_out; end
```

```
                3'b111 : begin a <= acc_out; end
```

```
                default : begin a <= 0; end
```

```
    endcase end
```

```
assign alu_out = a;
```

```
assign zr = &(a);
```

```
endmodule
```

```
e
```

## CODE FOR INPUT-OUTPUT BUFFER

```
module iobuffer(clk2,mrd,fch,alu_out,mdat);
```

```
input clk2,mrd,fch;
```

```
input [7:0] alu_out;
```

```
output [7:0] mdat;
```


```
wire en, en1;
```

```
assign en = mrd || fch || clk2;
```

```
assign en1 = ~en;
```


```
assign mdat = (en1) ? alu_out : 'hzz ;
```

```
endmodule
```

 
 
## CODE FOR ACCUMULATOR

```
module accum(clk, rst, alu_out, ldac, acc_out);  
  
  input clk, rst, ldac;  
  input [7:0] alu_out;  
  output [7:0] acc_out;      reg [7:0] acc_out;  
  
  always @ (posedge clk or negedge rst) begin  
    if (!rst) begin  
      acc_out <= 0;  
    end else if ( ldac == 1) begin  
      acc_out <= alu_out[7:0];  
    end  
  
  end  
endmodule
```



# CODE FOR MULTIPLEXER

```
module mux2_1(adir, adpc, fch, admem);  
  
  input [4:0] adir, adpc;          input fch;  
  output [4:0] admem;             reg [4:0] admem;  
  
  always @ (fch,adpc,adir) begin  
    case (fch)  
      1'b1 : admem = adpc;  
      1'b0 : admem = adir;  
    endcase end  
endmodule
```

# TESTBENCH CODE

```
module testbench();
```

```
    reg clk, rstreq, ewr;           reg [4:0] ead;       reg [7:0] edat;  
    wire zr;           int i;
```

```
topmodule dut11(clk,rstreq,ewr,ead,edat,zr);
```

```
    initial begin
```

```
        rstreq = 1;
```

```
        #12; @(negedge clk); rstreq = 0;
```

```
        #12; ewr = 1'd1;
```

```
        #12; ead = 5'd1;
```

```
    //int i ; //repeat(31) begin
```

```
endmodule
```